

**Sub: Digital Logic**

**1. Which one of the following logic expression is incorrect?**

1.  $1 \oplus 1 \oplus 0 = 1$       3.  $1 \oplus 0 = 1$   
2.  $1 \oplus 1 = 0$       4.  $1 \oplus 1 \oplus 1 = 1$

**Option:4**

**2.The time required for a gate or inverter to change its state is called**

1. Decay time  
2. Rise time  
3. Charging time  
4. Propagation time

**Option:4**

**3.The number of canonical expressions that can be developed over a 3-valued Boolean algebra is**

1. 16  
2. 8  
3. 64  
4. 32

**Option:3**

**4. What is the minimum number of two-input NAND gates used to perform the function of two input OR gate ?**

1. two  
2. one  
3. four  
4. three

**Option:4**

**5. How many 1's are present in the binary representation of  $15 \times 256 + 5 \times 16 + 3$  is**

1. 9  
2. 8  
3. 11  
4. 7

**Option:2**

**6. The time required for a pulse to change from 10 to 90 percent of its maximum value is called**

1. Decay time  
2. Rise time  
3. Charging time  
4. Propagation time

**Option:2**

**7.The output of NOR gate is**

1. Low if all of its inputs are low
2. High if all of its inputs are high
3. High if only of its inputs is low
4. High if all of its inputs are low

**Option:4**

**8.Which of the following adders can add three or more numbers at a time ?**

1. Carry-look-ahead adder
2. Parallel adder
3. Full adder
4. Carry-save-adder

**Option:4**

**9.The output of NOR gate is**

1. Low if all of its inputs are low
2. High if all of its inputs are high
3. High if only of its inputs is low
4. High if all of its inputs are low

**Option: 4**

**10.Which of the following adders can add three or more numbers at a time ?**

1. Carry-look-ahead adder
2. Parallel adder
3. Full adder
4. Carry-save-adder

**Option:4**

**11. In a digital counter circuit feedback loop is introduced to**

- A.Improve distortion
- B.Improve stability
- C.Reduce the number of input pulses to reset the counter
- D.Asynchronous input and output pulses

**Option: C**

**12..Select the statement that best describes the parity method of error detection:**

- A. Parity checking is best suited for detecting double-bit errors that occur during the transmission of codes from one location to another.
- B. Parity checking is not suitable for detecting single-bit errors in transmitted codes.
- C. Parity checking is best suited for detecting single-bit errors in transmitted codes.
- D. Parity checking is capable of detecting and correcting errors in transmitted codes.

Option C

13. A logic circuit that provides a HIGH output for both inputs HIGH or both inputs LOW is a(n):

A. Ex-NOR gate

B. OR gate

C. Ex-OR gate

D. NAND gate

Option A

14. A logic circuit that provides a HIGH output if one input or the other input, but not both, is HIGH, is a(n):

A. Ex-NOR gate

B. OR gate

C. Ex-OR gate

D. NAND gate

Option C

15. Identify the type of gate below from the equation  $X = A \oplus B = \bar{A}B + A\bar{B}$

A. Ex-NOR gate

B. OR gate

C. Ex-OR gate

D. NAND gate

Option C

16. How is odd parity generated differently from even parity?

A. The first output is inverted.

B. The last output is inverted.

Option B

17. How many 3-line-to-8-line decoders are required for a 1-of-32 decoder?

A. 1


B.

C. 4

D. 8


Option C

 18. Which of the figures shown below represents the exclusive-NOR gate?



Answer: Option B

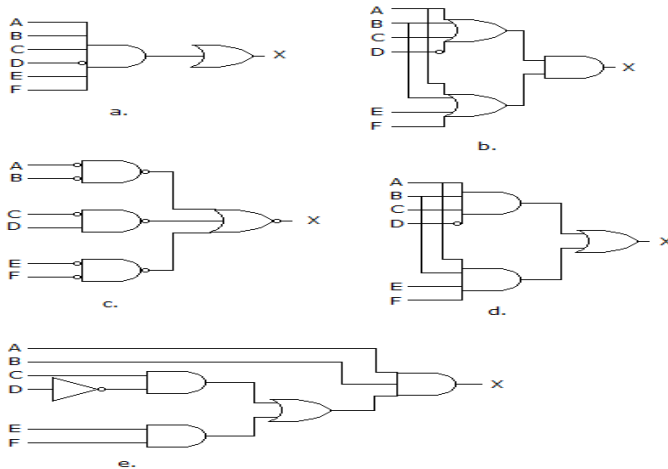19. Which of the circuits in figure (a to d) is the sum-of-products implementation of figure (e)?



Option D

20. Which statement BEST describes the operation of a negative-edge-triggered D flip-flop?

- A. The logic level at the  $D$  input is transferred to  $Q$  on NGT of  $CLK$ .
- B. The  $Q$  output is ALWAYS identical to the  $CLK$  input if the  $D$  input is HIGH.
- C. The  $Q$  output is ALWAYS identical to the  $D$  input when  $CLK = PGT$ .
- D. The  $Q$  output is ALWAYS identical to the  $D$  input.

Option A

21. How is a  $J$ - $K$  flip-flop made to toggle?

- A.  $J = 0, K = 0$
- B.  $J = 1, K = 0$
- C.  $J = 0, K = 1$
- D.  $J = 1, K = 1$

Option D

22. How many flip-flops are in the 7475 IC?

A.1

B.2

C.4

D.8

Option C

23.How many flip-flops are required to produce a divide-by-128 device?

A.1

B.4

C.6

D.7

Option D

24.How many flip-flops are required to make a MOD-32 binary counter?

A.3

B.45

C.5

D.6

Option C

25.How can a digital one-shot be implemented using HDL?

A.By using a resistor and a capacitor

B.By applying the concept of a counter

C.By using a library function

D.By applying a level trigger

Option B

26.The output of an exclusive-NOR gate is 1. Which input combination is correct?

A.A = 1, B = 0

B.A = 0, B = 1

C.A = 0, B = 0

D.none of the above

Option C

27.If a 3-input NOR gate has eight input possibilities, how many of those possibilities will result in a HIGH output?

A.1

B.2

C.7

D.8

Option A

28.If a signal passing through a gate is inhibited by sending a LOW into one of the inputs, and the output is HIGH, the gate is a(n):

A.AND

B.NAND

C.NOR

D.OR

Option B

**29. What is the minimum number of two-input NAND gates used to perform the function of two input OR gate ?**

**A. one**

**B. two**

**C. three**

**D. four**

**Option: C**

**30. The schmitt trigger may be used to?**

**[A] change voltage to corresponding frequency**

**[B] Change frequency to voltage**

**[C] Square slowly varying input**

**[D] None of above**

**Option:C**

**2. Which of the following is minimum error code?**

**[A] Octal code**

**[B] Grey code**

**[C] Binary code**

**[D] Excess 3 code**

**Option:B**

**31. Popular application flip-flop are ?**

**[A] Counters**

**[B] Shift registers**

**[C] Transfer registers**

**[D] All of above**

**Option:D**

**32.** SR Flip flop can be converted to T-type flip-flop if ?

[A] S is connected to Q

[B] R is connected to Q

[C] Both S and R are shortend

[D] S and R are connected to Q and Q' respectively

**Option: D**

**33.** Register is a ?

[A] Set of capacitor used to register input instructions in a digital computer

[B] Set of paper tapes and cards put in a file

[C] Temporary storage unit within the CPU having dedicated or general purpose use

[D] Part of the auxiliary memory

**Option:C**

**34.** For which of the following flip-flop the output clearly defined for all combinations of two inputs?

[A] Q type flip-flop

[B] R S type flip-flop

[C] J K flip-flop

[D] T flip-flop

**Option:C**

**35.** A simple flip-flop

[A] is 2 bit memory

[B] is 1 bit memory

[C] is a four state device

[D] has nothing to do with memory

**Option:B**

**36.** An SR flip flop cannot accept the following input entry

[A] Both input zero

[B] zero at R and one at S

[C] zero at S and one at R

[D] Both inputs one

**Option:D**

**37.** The main difference between JK and RS flip-flop is that?

[A] JK flip-flop does not need a clock pulse

[B] there is feedback in JK flip-flop

[C] JK flip-flop accepts both inputs as 1

[D] JK flip-flop is acronym of junction cathode multivibrator

**Option:C**

**38.** Radix of binary number system is \_\_\_\_\_?

[A] 0

[B] 1

[C] 2

[D] A & B

**Option:C**

**39.What is the minimum number of two-input NAND gates used to perform the function of two input OR gate?**

- A) 2      B) 1    C) 4    D) 3

**Option:D**

**40 . If  $A \oplus B = C$ , then**

- A)  $B \oplus C = A$       C)  $A \oplus C = B$   
B)  $A \oplus B \oplus C = 0$     D) All of these

**Option: A**

**41. How many truth tables can be made from one function table ?**

- A) Two                  B) One  
C) Any numbers      D) Three

**Option:A**

**42 which of the following is fastest Logic family**

- A) TTL                  C) ECL  
B) DTL                  D) CMOS

**Option:C**

**43 CMOS stands for**

- A. Complementary metal oxide semiconductors    B. Compulsory metal oxide semiconductors  
C. Complementary metal oxygen semiconductors                  D. NONE

**Answer    Complementary metal oxide semiconductors**

**44 The digital logic family which has minimum power dissipation is**

- A. TTL    B. RTL  
C. DTL    D. CMOS

**Answer CMOS**

**4 5 .The logic 0 level of a CMOS logic device is approximately**

- A. 1.2 volts    B. 0.4 volts



C. 5 volts

D. 0 volts

**Answer** 0 volts

46. CMOS circuits consume power

A. Equal to TTL

B. Less than TTL

C. Twice of TTL

D. Thrice of TTL

**Answer** Less than TTL

47. Which of the following logic families has the shortest propagation delay?

A. CMOS

B. TTL

C. ECL

D. 74SXX

**Answer** ECL

48. The output stage of most TTL logic is

A. To-tem pole

B. adder

C. push-pull

D. none

**Answer** To-tem pole

49. The following logic families have their propagation delay. Arrange them from lowest propagation delay to highest propagation delay. 1. TTL (Standard) 2. ECL 3. Low power CMOS 4. DTL

A. 2, 1, 4, 3

B. 2,4,1,3

C. 4,2,3,1

D. 1,2,3,4

**Answer** 2, 1, 4, 3

50. If the various logic families are arranged in the ascending order of their fan-out capabilities, the sequence will be

A. TTL, DTL, ECL, MOS

B. DTL, TTL, MOS, ECL

C. MOS, DTL, TTL, ECL

D. ECL, TTL, DTL, MOS

**Answer** MOS, DTL, TTL, ECL

51. Consider the following logic families & correct sequence of the logic families in the order of their increasing noise margin. 1. MOS 2. TTL 3. RTL 4. ECL

A. 3, 4, 1, 2

B. 3, 4, 2, 1

C. 4, 3, 2, 1

D. 4, 3, 1, 2

**Answer** 3, 4, 1, 2

52. Which is not a bipolar logic family?

A. TTL

B. ECL

C. IIL

D. NMOS

**Answer** NMOS

**53. Which logic family dissipates the minimum power?**

A. DTL

B. TTL

C. ECL

D. CMOS

**Answer: Option**

**54. Combinational logic circuit which is used to send data coming from a single source to two or more separate destinations is called as**

A. decoder

B. encoder

C. multiplexer

D. de-multiplexer

**Answer: Option D**

**55. What logic function is obtained by adding an inverter to the inputs of an AND gate?**

- A. OR
- B. NAND
- C. XOR
- D. NOR

**Answer: Option D**

**56. An OR gate has 6 inputs. How many input words are in its truth table?**

- A. 64
- B. 32
- C. 16
- D. 128

**Answer: Option A**

**57. Which of the following Boolean algebra statements represent commutative law**

- A.  $(A+B)+C=A+(B+C)$
- B.  $A.(B+C)=(A.B)+(A.C)$
- C.  $A+BB+A$
- D.  $A+AA$
- E. None of the above

**Answer: Option C**

**58. A multiplexer is also known as**

- A. coder
- B. decoder
- C. data selector
- D. multivibrator
- E. None of the above

**Answer: Option C**

**59. An AND gate has 7 inputs, what is the only input word that produces a 1 output?**

- A. 0
- B. 1111
- C. 1110000

D. 1111111

**Answer: Option D**

**60. The Gray code for decimal 7 is**

A. 111

B. 1011

C. 100

D. 101

**Answer: Option C**

61. Select the statement that best describes the parity method of error detection:

A. Parity checking is best suited for detecting double-bit errors that occur during the transmission of codes from one location to another.

B. Parity checking is not suitable for detecting single-bit errors in transmitted codes.

C. Parity checking is best suited for detecting single-bit errors in transmitted codes.

D. Parity checking is capable of detecting and correcting errors in transmitted codes.

**Answer: Option C**

62. A logic circuit that provides a HIGH output for both inputs HIGH or both inputs LOW is a(n):

A. Ex-NOR gate

B. OR gate

C. Ex-OR gate

D. NAND gate

**Answer: Option A**

63. A logic circuit that provides a HIGH output if one input or the other input, but not both, is HIGH, is a(n):

A. Ex-NOR gate

B. OR gate

C. Ex-OR gate

D. NAND gate

**Answer: Option C**

64. Identify the type of gate below from the equation  $X = A \oplus B = \bar{A}B + A\bar{B}$

A.Ex-NOR gate

B.OR gate

C.Ex-OR gate

D.NAND gate

**Answer: Option C**

65. How is odd parity generated differently from even parity?

A.The first output is inverted.

B.The last output is inverted.

Answer: Option B

A. Propagation delay in TTL is due to slow switching speeds.

A. True

B. False

**Answer** False

B. In TTL the noise margin is between 0.8 V and 0.4 V.

A. True

B. False

**Answer**True

C. CMOS has High speed as compared to TTL

A. True

B. False

**Answer** False

D. When using TTL logic to drive CMOS logic the high level voltage of the TTL output must be increased with a pull-up resistor.

A. True

B. False

**Answer** True

E. When the two logic families being interfaced have different power supplies then special circuits called level shifters or translators must be used.

A. True

B. False

**Answer** True

F. The CMOS family has high input impedance and very high power consumption.

A. True

B. False

**Answer** False

G. ECL IC technology is faster than TTL technology

A. True

B. False

**Answer** True

H. There are four different logic levels in TTL and CMOS:  $V_{IH}$ ,  $V_{IL}$ ,  $V_{OL}$ ,  $V_{OH}$

A. True

B. False

**Answer** True