 


# VHDL Introduction

---



# VHDL

---

- ◆ VHSIC Hardware Description Language
  - it *is* a programming language
  - it *is not* a programming language
    - » it's a hardware description language
- ◆ You *might* write a dBase program in VHDL
  - we will stick with *synthesizable* VHDL
    - » we want to build hardware in the end
    - » synthesis tools only take a subset of VHDL

# VHDL Elements

---

- comments look like this
- ◆ identifiers
- ◆ numbers
- ◆ characters: '0'
- ◆ strings: "0011" or "abc"

# VHDL Types

---

- ◆ integers
  - easily converted to bit strings and back
- ◆ floating point
- ◆ enumeration types
- ◆ arrays
- ◆ subtypes
  - restricted version of another type
    - » **subtype address is integer range 0 to 65535**

# Other VHDL Elements

---

- ◆ attributes
  - built-in
    - » clk'event
    - » vec'high
    - » xyz'range
  - user-defined
  - one way to give *synthesis directives*
- ◆ entities/architectures
- ◆ configurations

# Vector Types Tutorial

---

```
-- The std_logic_arith package defines the SIGNED and UNSIGNED types
-- In this architecture type conversions are used on plain
-- STD_LOGIC_VECTOR's to force them to be compared as SIGNED if an
-- UNSIGNED compare is not wanted.
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
entity demoB is
end;
architecture SIGNED_convert of demoB is
    signal a : STD_LOGIC_VECTOR(3 downto 0);
    signal b : STD_LOGIC_VECTOR(3 downto 0);
    signal c : STD_ULOGIC;
    signal d : STD_ULOGIC;
begin
    a <= "1111";
    b <= "0100";

    -- this is true, the type conversions make 'a' be viewed as a -1.
    c <= '1' when (SIGNED(a) < SIGNED(b)) else '0';
    -- this is false, STD_LOGIC_VECTORs are UNSIGNED by default.
    d <= '1' when (a < b) else '0';
end SIGNED_convert;
```

# Vector Types (part 2)

---

```
-- By using package std_logic_signed we force STD_LOGIC_VECTORs to be treated
-- as SIGNED by default. Type conversions are now needed to make them be treated as UNSIGNED.
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_signed.all;
entity demoC is
end;
architecture use_signed of demoC is
    signal a : STD_LOGIC_VECTOR(3 downto 0);
    signal b : STD_LOGIC_VECTOR(3 downto 0);
    signal c : STD_ULOGIC;
    signal d : STD_ULOGIC;
begin
    a <= "1111";
    b <= "0100";

    -- this is true, due to the extra USE stmt above
    c <= '1' when (a < b) else '0';
    -- this is false, the type conversions make 'a' be viewed as a 15.
    d <= '1' when (UNSIGNED(a) < UNSIGNED(b)) else '0';
end use_signed;
```

# Vector Types (part 3)

---

```
-- Using the SIGNED type it is also possible to have SIGNED without
-- type conversions.
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
entity demoD is
end;
architecture SIGNED_type of demoD is
    signal a : SIGNED(3 downto 0);
    signal b : SIGNED(3 downto 0);
    signal c : STD_ULOGIC;
begin
    a <= "1111";
    b <= "0100";

    -- this is true, due to their inherent types.
    c <= '1' when (a < b) else '0';
end SIGNED_type;
```



# Entity Declarations

---

```
entity add4 is                                -- 4 bit adder
  port(
    a : in std_logic_vector(3 downto 0);
    b : in std_logic_vector(3downto 0);
    s : out std_logic_vector(3downto 0));
end add4;
```

```
entity adder is                               -- generic adder
  generic (width: positive);
  port(
    a : in std_logic_vector(width-1 downto 0);
    b : in std_logic_vector(width-1 downto 0);
    s : out std_logic_vector(width-1 downto 0));
end adder;
```

# More Entity Declarations

---

```
entity adder is                                -- another generic adder
port(      a : in std_logic_vector;
           b : in std_logic_vector;
           s : out std_logic_vector);
end adder;

architecture foo of adder is
begin
    ... a'high ...
    ... b'range
end;

-- no ports, a container for a testBench
entity testBench is
end testBench;
```

# Architectures

---

- ◆ The *body* or *implementation* of the entity.
- ◆ Can have more than one
  - specify which one to use
    - » using configurations (ugh!)
    - » to the tool

# Architecture Examples

---

architecture first of add4 is

begin

s <= a + b; -- works with std\_logic\_vector or integer

end;

architecture second of add4 is

signal c: std\_logic\_vector(2 downto 0);

begin

s(0) <= a(0) XOR b(0);

c(0) <= a(0) AND b(0);

s(1) <= a(1) XOR (b(1) XOR c(0));

c(1) <= .....

end add4;

# Yet More on Architectures

---

## ◆ local declarations

- types
- constants
- signals (wires)

## ◆ Examples:

- subtype addr is ...
- constant a : integer := 12;
- signal d : bit := '0';

# Concurrent Statements

---

◆  $s(0) \leq a(0) \text{ XOR } b(0);$

◆  $q \leq a \text{ when } sel='0' \text{ else } b;$

◆  $\text{process}(a, b, sel)$   
begin  
  if  $sel='0'$  then  
     $q \leq a;$   
  else  $q \leq b;$   
end process;

Each of these lines executes  
any time one of its inputs  
changes...  
(what are its inputs?)

A process is like one big  
concurrent statement. It executes  
whenever one of its inputs  
changes...  
(what are its inputs?)

It executes sequentially once it is  
awakened for execution.

◆ **always concurrently executing**

# Concurrent vs. Sequential Code

---

## ◆ Sequential Code

- processes
- procedures
- functions

For *every* concurrent signal assignment there is a corresponding sequential construct.

The opposite is NOT true.

## ◆ Concurrent Code

- assignments
  - » simple
  - » conditional
  - » selected

# Example Assignments

---

**a <= b;**

**q <=        a when sel="00" else  
             b when sel="01" else  
             c when sel="10" else  
             d;**

**process(b)  
begin  
  a <= b;  
end process;**

**process(a, b, c, d, sel)  
begin  
  if sel = "00" then  
    q <= a;  
  elsif sel = "01" then  
    q <= b;  
  elsif sel = "10" then  
    q <= c;  
  else  
    q <= d;  
  end if;  
end process;**



# More Assignments

---

with sel select

```
q <= a when "00" else
    b when "01" else
    c when "10" else
    d;
```

process(a, b, c, d, sel)

```
begin
case sel is
    when "00" => q <= a;
    when "01" => q <= b;
    when "10" => q <= c;
    when others => q <= d;
end case;
end process;
```

# Synthesis Note

---

- ◆ As much as you don't want to...
  - think hardware in your head
  - “Just what will this construct synthesize to”
- ◆ NOT a general programming language
  - recursion???

# What in the world is this?

---

```
process(b)
begin
  for i in b'range loop
    a(i) <= not(b(i));
  end loop;
end process;
```

- ◆ It's just a shorthand for: **a <= not(b)**; where a and b are vectors.
  - No timing or sequentiality is implied!!!

# Processes

---

- ◆ Code executes sequentially
  - last assignment to a signal takes precedence
  - can have **wait()** statements
    - » useful for synchronous logic

# A Loadable Register

---

```
process(clk, load, dataIn)
begin
  if clk'event and clk = '1' then
    if load = '1' then
      dataOut <= dataIn;
    end if;
  end if;
end process;
```

- ◆ What happens when load='0'???

# Synthesis Note

---

- ◆ Use synthesizable idioms
  - synthesizers are not going to recognize just anything
  - SYNOPSYS VHDL Programming Guide
    - » lists their idioms

# A Clearable, Loadable Register

---

```
process(clk, load, clr, dataIn)
begin
  if clk'event and clk = '1' then
    if load = '1' then
      dataOut <= dataIn;
    elsif clr = '1' then
      dataOut <= (others => '0');
    end if;
  end if;
end process;
```

-- this is a synchronous clear!  
-- all zeroes!

- ◆ Which takes priority?
- ◆ How to write it so they have equal priority? (be careful!!!)

## #2 Clearable, Loadable Register

---

```
process(clk, load, clr, dataIn)
begin
  if clk'event and clk = '1' then
    if load = '1' then
      dataOut <= dataIn;
    end if;
    if clr = '1' then
      dataOut <= (others => '0');
    end if;
  end if;
end process;
```

◆ Which takes priority?




# Synthesis Note

---


- ◆ If priority NOT inferred a MUX results.
- ◆ If priority inferred, extra logic results.
 
```
if sel="00" then ...  
elsif sel="01" then ...  
elsif sel="10" then...  
else ...
```



Is priority inferred?  
...really?
 
```
if load = '1' then ...  
elsif clr = '1' then ...
```



If you *know* they are mutually exclusive  
then you can tell SYNOPSIS to do a MUX...

Getting complicated if-then-elses right can be a nightmare... (maybe you want a case)

# FSM Design - Moore Machine

---

```
IFL: process(currentState, in1, in2)
begin
  nextState <= currentState; -- default
case currentState is
  when stateA =>
    nextState <= stateY;
  when stateB =>
    if in1='0' AND in2='1' then
      nextState <= stateC;
    else nextState <= stateD;
    end if;
end case;
end process;
```

```
OFL: process(currentState)
begin
  out1 <= '0';           -- default value
case currentState is
  when stateA =>
    out1 <= '1';
  when stateB =>        ..
  when stateC =>        ...
end case;
end process;
```

```
stateReg: process(clk)
begin
  if clk'event and clk = '1' then
    currentState <= nextState;
  end if;
end process;
```

How would you code IFL and OFL in same process?

# FSM Design - Mealy Machine

---

```
IFL: process(currentState, in1, in2)
begin
  nextState <= currentState; -- default
  out1 <= '0';                -- default
  case currentState is
    when stateA =>
      nextState <= stateY;
      out1 <= '1';
    when stateB =>
      if in1='0' AND in2='1' then
        nextState <= stateC;
        out1 <= '1';
      else nextState <= stateD;
      end if;
    end case;
  end process;
```

```
stateReg: process(clk)
begin
  if clk'event and clk = '1' then
    currentState <= nextState;
  end if;
end process;
```

# Mealy Machine - Are You Sure?

---

```
IFL: process(currentState, in1, in2)
begin
  nextState <= currentState; -- default
  out1 <= '0';
  case currentState is
    when stateA =>
      nextState <= stateY;
      out1 <= '1';
    when stateB =>
      if in1='0' AND in2='1' then
        nextState <= stateC;
        out1 <= '1';
      else nextState <= stateD;
      end if;
    end case;
  end process;
```

```
stateReg: process(clk)
begin
  if clk'event and clk = '1' then
    currentState <= nextState;
  end if;
end process;
```


I lied, it is a *mixed* machine.  
Is there anything wrong with this?  
Nope...

# FSM Design

---

- ◆ Use enumerated types for states
- ◆ Code in (at least) two processes
  - combinational
    - » mix Mealy and Moore - depending on timings
  - next state register

# UART Block Diagram

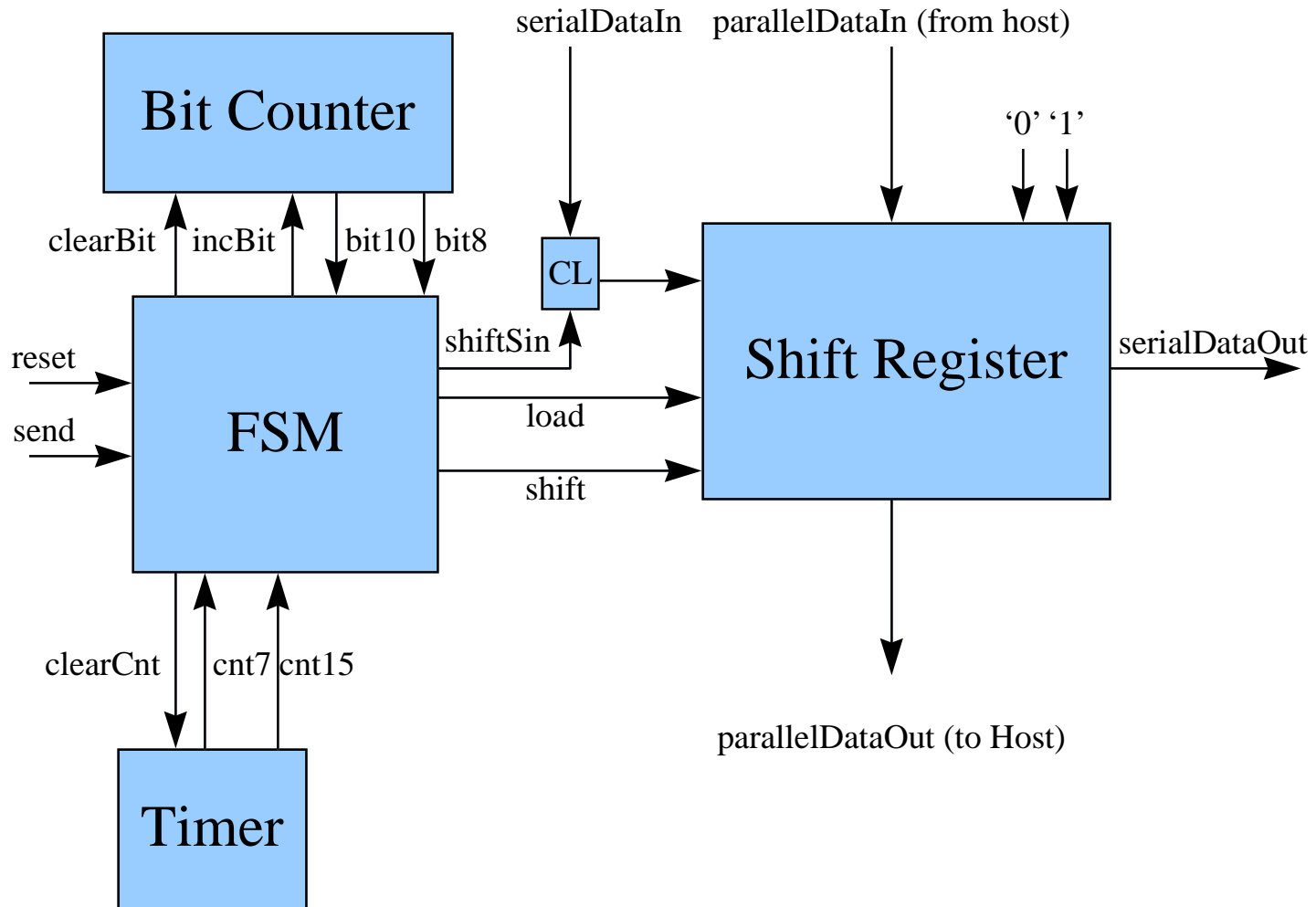

# The UART Design - One Method

---

architecture first of UART is

signal ...;

begin

comb: process(...)

comb2: process(...)

nextstate: process(...)

shift: process(...)

parity: process(...)

bitCount: process(...)

timer: process(...)

end first;

The FSM input forming logic  
The FSM output forming logic

The FSM state register

The PISO/SIPO shift register

The parity generator (combinational)

The bit counter and divide down timers

# How About Hierarchy?

---

architecture hierarchical of add4

signal c : bit\_vector(3 downto 0);

signal gnd : bit;

component adder

port (a : in bit; b : in bit; cin : in bit; s : out bit; cout : out bit);

end component;

for all:adder use entity work.add(gates); -- Tell simulator which one to use

begin

gnd <= '0'; -- GND not needed in VHDL 92 (which we don't have yet)

X0: adder port map (a => a(0), b => b(0), cin => gnd, s => s(0), cout => c(0));

X1: adder port map (b => b(1), cin => c(0), s => s(1), a => a(1), cout => c(1));

X2: adder port map (a(2), b(2), c(1), s(2), c(2));

X3: adder port map (a => a(3), b => b(3), cin => c(2), s => s(3), cout => c(3));

end hierarchical;

- Note all the different ways to specify parameter lists...



# Hierarchy with Generates

---

architecture gen of add4 is

... put component decl here...

begin

**G0: for i in 0 to 3 GENERATE**

if i=0 then

X: adder port map (a => a(0), b => b(0); cin => gnd; s => s(0); cout => c(0));

else

Y: adder port map (a => a(i), b => b(i); cin => c(i-1); s => s(0); cout => c(i));

end if;

**END GENERATE;**

-- Don't quote me on the syntax...

# Hierarchy - contd.

---

- ◆ Can put all configurations in a separate file
  - SYNOPSIS ignores them all anyway
    - » uses last analyzed architecture for each entity
- ◆ Can pass in generics
  - define widths or other numeric values

# My Coding Style

---

- ◆ Use hierarchy (structural design) for highest levels
  - chip, datapath, control
- ◆ Use behavioral design for lowest levels
  - counters, shifters, arithmetic
- ◆ Don't use hierarchy for things like counters, shifters, ...
  - rarely want exactly the same thing twice
  - get what you *really* want in every case
  - typing the code is often easier than component + instantiation
- ◆ Design from the top-down (in my head)
- ◆ Develop code from the bottom-up (in editor)

# Synthesis Notes

---

- ◆ The synthesizer will optimize every block in its environment
  - timings of arriving inputs
  - demands on timings of outputs
  - loading dependent
- ◆ Using hierarchy for small pieces may not save much
- ◆ SYNOPSIS does well on up to about 5K gates in a block
  - if bigger than that, try again...

# Synthesis Notes

---

- ◆ Synthesizer will choose *smallest* implementation that meets timing
- ◆ Synthesis script is where you tell it the target speed and input arrival times.
- ◆ Must design according to recommendations
  - else it will get confused


# Synthesis Notes

---

- ◆ Must design according to some recommendations they provide
  - else it will not give you an optimal solution

# Synthesis Notes: Timing Analysis

---

 

What is arrival time of signal X?  $\text{clk-Q} + \text{wiring\_delay}$ .

Put FF as last element (if possible) in module to simplify analysis.  
Avoid combinational-only modules (if possible).

# VHDL Simulation Timing Model

---

- ◆ Real timing

**a <= b after 12.6 ns;**

- ◆ Unit delay timing

**a <= b;**

**c <= a;**

Which value of a does c get?



# Unit Delay Simulation

---

```
simulate() {  
  repeat {  
    flag = 0;  
    for_each_signal_S_on_changed_list {  
      for_each_signal_T_on_S's_fanout_list {  
        newT = compute_new_value(T)  
        if newT != T {  
          flag = 1;  
          put_T_on_changed_list;  
        }  
      }  
    }  
    remove_S_from_changed_list;  
  }  
  } (until flag = 0);  
}
```

A breadth-first traversal -  
maintains order.

No timing information.

Concludes when one pass  
through circuit results in  
an empty changed list.

# Timing Simulation

---

- ◆ Instead of a changed\_list
  - sorted event list
- ◆ When a signal changes in +5ns --
  - record that in event list
- ◆ Make events happen at proper times

# VHDL Timing - does both

---

- ◆ all signals assignments take one  $\Delta$  delay if no time specified

a <= b;

c <= a;                      -- c gets *old* value of a

- ◆ process repeats until circuit stabilizes
  - in unit delay mode
- ◆ time then advances to the next timed event

# $\Delta$ Delay Timings

---

- ◆ *All* signal assignments take one  $\Delta$ 
  - unless an actual delay is specified
  - this is true in concurrent code
  - this is true in sequential (process) code
  - can be VERY confusing

# Example of $\Delta$ Timing Subtleties

---

```
process(clk)
begin
  if clk'event and clk = '1' then
    a <= b;
    b <= a;
  end if;
end process;
```

- So, what does the above code do?
    - both a and b could end up with the original b value
  - OR
  - a and b could get swapped...
- which is it???? what does the hardware look like????

# More $\Delta$ Timing Subtleties

---

architecture deltaProblems of classExample is

begin

a <= b when ctl = '1';

b <= a when ctl = '1';

end deltaProblems;

- So, what does the above code do?
  - a and b could get swapped...
- OR
- ????

# VHDL Timing: Do you use both?

---


- ◆ Not really - if you are synthesizing
  - synthesizers ignore timing specifications in code
  - you give synthesizers target timings as a part of the synthesis process, NOT in the VHDL code

- ◆ BUT - your testbench will use it:

<code>clk &lt;= not(clk) after 10 ns;</code>	-- a 50 MHz square wave
<code>reset &lt;= '0', '1' after 25 ns, '0' after 50 ns;</code>	-- a reset pulse

# VHDL Testbenches

---

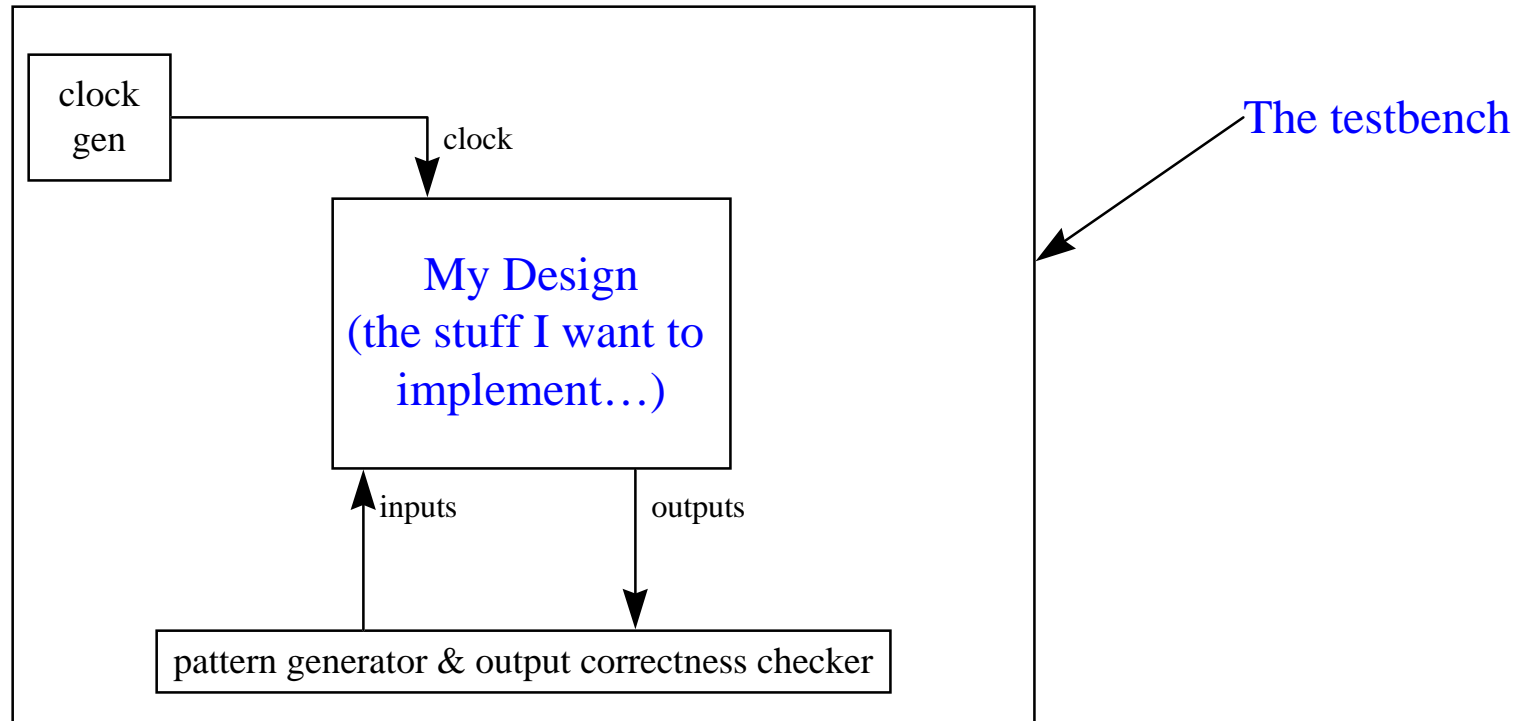

- Patterns can be generated algorithmically or read from a file
- Comparing to correct values is optional (can just view waveforms in simulator instead)
- Correct values to compare against can be generated algorithmically or from file...



# Testbench Creation

---

- ◆ Create a nice general testbench
  - inputs come from an array of 1's and 0's
  - inputs come from a file
- ◆ Cannibalize it for all simulations you do

# Variables

---

- ◆ Declared local to a process
- ◆ Use `:=` to assign to
- ◆ Happens immediately, like in C code
  - no  $\Delta$  delay
- ◆ Note in your text how they are often used

# An Example With Variables

---

```
patternGenerator process
```

```
  variable cnt : integer := 0; ← A variable declaration
```

```
  begin
```

```
    for i in 0 to 9 loop
```

```
      wait until (clk'event and clk='1');
```

```
      cnt := cnt + 1; ← Increment it.
```

```
      some_signal <= cnt; ← Assign it to some variable.
```

```
    end loop;
```

```
  end process;
```

(It holds a value just like a signal - it just cannot be used outside the process and has a zero-delay assignment.)

# More on Processes

---

- ◆ A process executes once on startup

- ◆ A process must have one of:

- sensitivity list
- wait statement

`process(a, b, c)`

`process`

`begin`

`wait until clk'event and clk='1'`

`do_something_here;`

`end process`

There is an implied loop in the *wait* version

# Final Thoughts

---

- ◆ Best way to learn VHDL is to write and simulate VHDL modules...
- ◆ Next best way is to study existing code...
  - SYNOPSYS manuals
  - Splash2 models